

Type 5. Application to electrical circuit.

$$\rightarrow I = \frac{dq}{dt}$$

$$q = \int i \cdot dt$$

voltage drop across the resistance = Ri

the Inductance $L = L \frac{di}{dt}$

the capacitance $C = \frac{q}{\epsilon}$

* Kirchhoff's law, the algebraic sum of voltage around any closed ckt = Resultant EMF in ckt


* The algebraic sum of current flowing into any terminal is zero

* Differential Equation

a) Consider a ckt containing resistance R and Inductance L in series with


E or then

b) By Kirchhoff's law

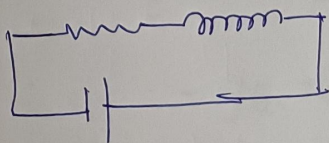

$$Ri + L \frac{di}{dt} = E$$

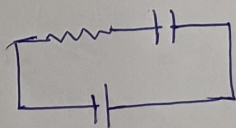b) Consider a ckt containing resistance R and capacitance C in series with voltage drop EMF E .



By Kirchhoff's law, $Ri + \frac{q}{C} = E$

$$R \cdot \frac{dq}{dt} + \frac{q}{C} = E$$

$$\begin{aligned} \int e^{at} \sin bt \cdot dt &= \frac{e^{at}}{a^2 + b^2} (a \sin bt - b \cos bt) \\ &= \frac{e^{at}}{\sqrt{a^2 + b^2}} \left(\frac{a}{\sqrt{a^2 + b^2}} \sin bt - \frac{b}{\sqrt{a^2 + b^2}} \cos bt \right) \end{aligned}$$

$$= \frac{e^{at}}{\sqrt{a^2+b^2}} (\sin bt \cos \phi - \cos bt \sin \phi)$$

$$= \frac{e^{at}}{\sqrt{a^2+b^2}} \sin(bt - \phi)$$

$$\text{take } \cos \phi = \frac{a}{\sqrt{a^2+b^2}}$$

$$\sin \phi = \frac{b}{\sqrt{a^2+b^2}}$$

$$\therefore \tan \phi = \frac{b}{a}$$


$$\phi = \tan^{-1}\left(\frac{b}{a}\right)$$

$$\int e^{at} \cos bt = \frac{e^{at}}{a^2+b^2} (a \cos bt + b \sin bt)$$


$$= \frac{e^{at}}{\sqrt{a^2+b^2}} \cos(bt - \phi)$$

$$\phi = \tan^{-1}\left(\frac{b}{a}\right)$$

$$Ri + L \frac{di}{dt} = E$$

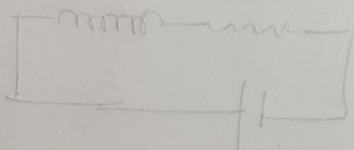

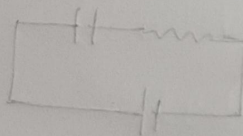Consider a ckt containing resistance R and inductance L in series with voltage drop E.



$$Ri + \frac{q}{C} = E$$

$$R \frac{dq}{dt} + \frac{q}{C} = E$$

$$\int e^{at} \sin bt = \frac{e^{at}}{a^2+b^2} (\cos bt - \sin bt)$$

The equation of emf in terms of current i for electrical ckt having resistance r and condenser of capacity C in series is $E = Ri + \int \frac{i}{C} dt$
 find current i at any time t when $E = E_0 \sin \omega t$

Given: $E = Ri + \int \frac{i}{C} dt$

$$E_0 \sin \omega t = Ri + \int \frac{i}{C} dt$$

diff w.r.t t .

$$\frac{E_0 \cos \omega t \cdot \omega}{1} = R \frac{di}{dt} + \frac{i}{C}$$

dividing by R

$$\frac{d i}{d t} + \frac{1}{RC} i = \frac{E_0 \omega \cos \omega t}{R}$$

which is linear in i

$$P = \frac{1}{RC}, \quad Q = \frac{E_0 \omega \cos \omega t}{R}$$

$$I.f. = e^{\int \frac{1}{RC} dt} = e^{t/RC}$$

- Soln, $i \cdot I.f. = \int Q \cdot I.f. dt + C$

$$i e^{t/RC} = \int \frac{E_0 \omega \cos \omega t}{R} e^{t/RC} dt + C$$

$$i e^{t/RC} = \frac{E_0 \omega}{R} \int e^{t/RC} \cos \omega t dt$$

$$i e^{t/RC} = \frac{E_0 \omega}{R} \frac{e^{t/RC}}{\sqrt{\frac{1}{R^2 C^2} + \omega^2}} \cdot \cos(\omega t - \phi) + C \quad \phi = \tan^{-1}(\omega RC)$$

In ckt containing inductance L , resistance R , voltage E and diff. eqⁿ is

$$E = Ri + L \frac{di}{dt}$$

also given, $L = 640 \text{ Hen}$

$$R = 250 \Omega$$

$$E = 500 \text{ V}$$

1) the current i being zero when $t=0$ find time that lapses before it reaches 90% of its maximum value.

2) Show that the current will approach to 2 Amp, when $T \rightarrow \infty$

$$\Rightarrow L \frac{di}{dt} + Ri = E$$

$$\frac{di}{dt} + \frac{Ri}{L} = \frac{E}{L} \text{ which is linear in } i$$

$$P = \frac{R}{L}, \quad Q = \frac{E}{L}$$

$$I.F. = e^{\int \frac{R}{L} dt}$$

$$I.F. = e^{\frac{Rt}{L}}$$

$$\text{Sol}^n, \quad i \cdot I.F. = \int Q \cdot I.F. dt + C$$

$$i e^{\frac{Rt}{L}} = \int \frac{E}{L} \cdot e^{\frac{Rt}{L}} dt + C$$

$$i e^{\frac{Rt}{L}} = \frac{E}{L} \cdot \frac{L}{R} e^{\frac{Rt}{L}} + C$$

$$i e^{\frac{Rt}{L}} = \frac{E}{R} e^{\frac{Rt}{L}} + C$$

$$i = \frac{E}{R} + \frac{C}{e^{\frac{Rt}{L}}} \quad \text{--- (1)}$$

given that at $t=0$, $i=0$.

$$0 = \frac{E}{R} + C$$

$$C = -\frac{E}{R}$$

$$\text{from (1)} \quad i = \frac{E}{R} - \frac{E}{R} e^{-\frac{Rt}{L}} \quad \text{--- (2)}$$

Eqn 13

maximum value of i is i_{max} which is obtain at $t \rightarrow \infty$

$$i_{max} = \frac{E}{R}$$

we have to find time t when current reaches to 90% of its max value

$$i = \frac{90}{100} \times i_{max} = \frac{9E}{10R}$$

Eqn 2 becomes.

$$\frac{9E}{10R} = \frac{E}{R} - \frac{E - RE/L}{e^{Rt/L}}$$

$$e^{Rt/L} = \frac{1}{10}$$

$$-Rt/L = \log 10^{-1}$$

$$\frac{Rt}{L} = \log 10$$

$$t = \frac{L}{R} \log 10$$

$$t = 5.89$$

$$t \rightarrow \infty \quad i = i_{max}$$

$$i = \frac{E}{R} = \frac{500}{250} = 2A$$

3 At 200 Ω resistance is connected in series with $C = 0.001 \text{ F}$ and
 Emf $E = 400 \times e^{-3t}$. if $Q = 0$ at $t = 0$ find time t
 when max charge is on the capacitor.

→ Here, the ckt contains Resistance R and cap C .
 By Kirchhoff's law, voltage law across $R = Ri$
 across $C = \frac{q}{C} = \frac{400e^{-3t}}{C}$

$$Ri + \frac{q}{C} = 400e^{-3t}$$

put $R = 200$, $C = 0.001 \times 10^{-3}$.

$$200 \frac{dq}{dt} + \frac{q}{0.001} = \frac{400e^{-3t}}{0.001}$$

$$\frac{dq}{dt} + 5q = 2e^{-3t}$$

$p = 5$ $Q = 2e^{-3t}$

$$I.f. = e^{\int 5 \cdot dt} = e^{5t}$$

Soln. $q \cdot I.f. = \int \frac{2e^{-3t}}{e^{5t}} e^{5t} \cdot dt + K \cdot \frac{400}{0.001} = \frac{2}{2} = 1$

$$qe^{5t} = e^{2t} + K$$

$$q = e^{-3t} + Ke^{-5t}$$

when $t = 0$ $q = 0$

$$0 = 1 + K$$

$$K = -1$$

$$\therefore q = e^{-3t} - e^{-5t} \quad \text{--- (1)}$$

for max charge $\frac{dq}{dt} = 0$

$$\therefore \frac{dq}{dt} = -3e^{-3t} + 5e^{-5t} = 0$$

$$\frac{3}{5} = e^{-2t}$$

$$t = \frac{1}{2} \log \left(\frac{5}{3} \right)$$